

# Verilog Lab II



# State machines

- A description of the design functionality will be provided.
- The objective is to translate the description into a synthesizable Verilog code.
- Use the module interface that will be provided.
- To do a syntax check on the Verilog code written, **vlogan** tool can be used.

```
vlogan -sverilog -debug_access+all verilog_file.v
```

- You can compile the simulation executable with


```
vcs -sverilog -debug_access+all -kdb +memcbk verilog_file.v
```

- Then start the simulation with

```
./simv -verdi
```
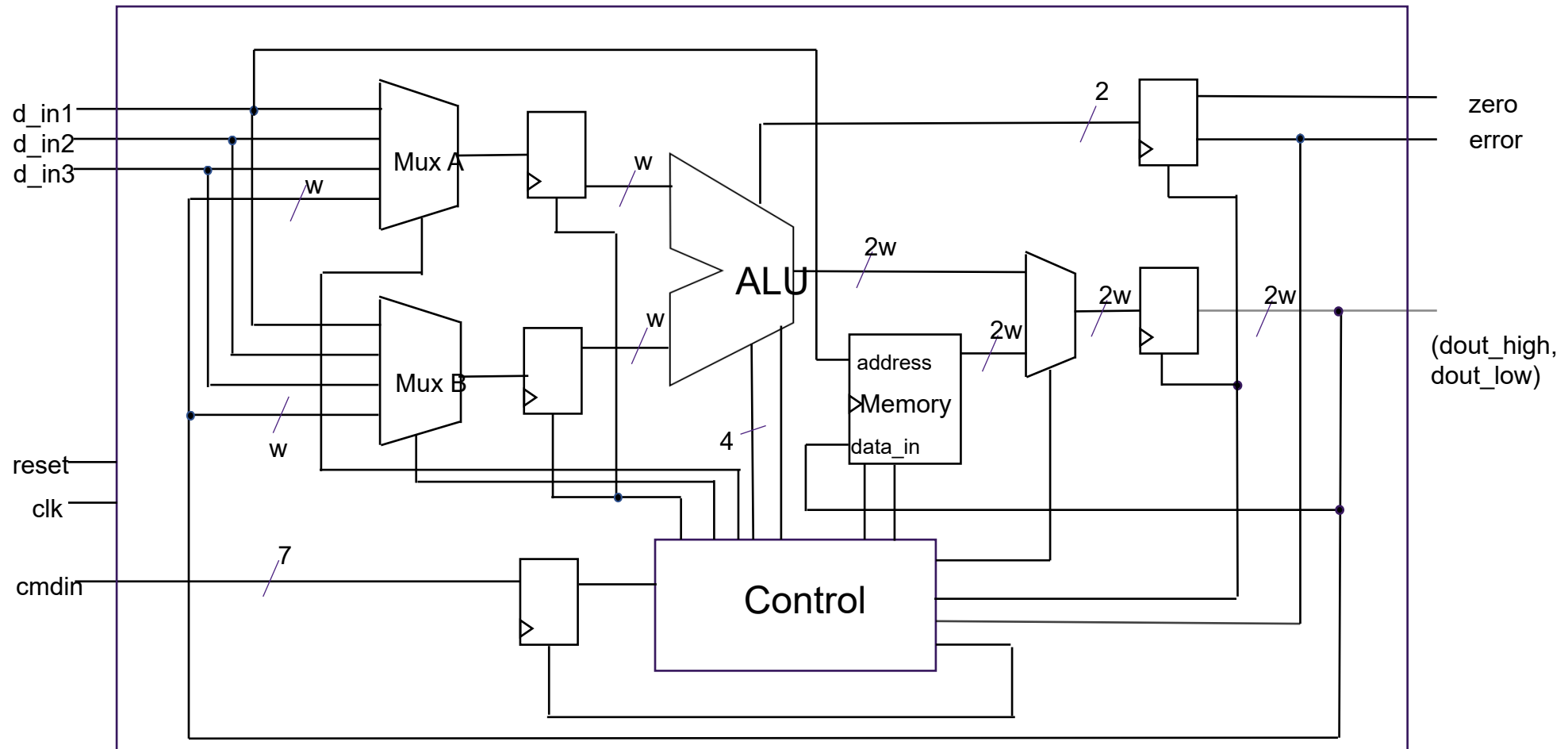
# Full CPU design

- The objective is to create a basic multicycle processor as shown in the diagram below.
  - Modules previously designed should be used. (Mux, ALU, Regbank)




# Full CPU design

- Specifications of the design:
  - This is a multicycle processor (3 stages) with no pipelining.
  - It has 3 variable with input buses to be used as operands.
  - The **ALU** has 2 multiplexed inputs:
    - Each **MUX** is feed by the 3 input buses and the **ALU** output.
    - Details on how to control the **ALU** are available in Lab 2d.
  - Both reset (**rst**) and clock (**clk**) signals should be connected to every module that uses them.
  - It has a control unit feed by a 6 bit word (**cmdin**). This control unit has to:
    - Enable the register stages only when applicable
    - Select the outputs of each **MUX**
    - Provide the control signals for the **ALU**.
      - Inverted valid data signal must be asserted when data is feed from the feedback loop and the previous result was not valid (**Error** condition)
      - **OPCODE** to select the operation performed by the **ALU**.
 
# Full CPU design

- The **control** block shall be designed to implement the following Instruction Set Architecture (ISA):



- The **opcode** bus should be decoded according to the following table:

opcode[2]	opcode[1]	opcode[0]	Operation
0	0	0	Add
0	0	1	Sub
0	1	0	Mul
0	1	1	Div
1	0	0	NOP
1	0	1	Load
1	1	0	Store
1	1	1	NOP

# Full CPU design

- The control module
  - Write the Verilog code for implementing this module based on the details and ISA provided previously.
  - Write a test bench to validate this module. It should cover all possible operations, corner cases and exercise all outputs.
  - Its interface should be as follows:

```
module control (  
    input clk,  
    input rst,  
    input [6:0] cmd_in,  
    input p_error,  
    output aluin_reg_en,  
    output datain_reg_en,  
    output memoryWrite, memoryRead, selmux2,  
    output aluout_reg_en,  
    output nvalid_data,  
    output [1:0] in_select_a,  
    output [1:0] in_select_b,  
    output [3:0] opcode  
);
```

# Full CPU design

- Full design

- Write the Verilog code that implements this simple microprocessor. At this point it is mostly about connecting together all the modules created so far.
- A test bench will be provided.
- Its interface should be as follows

```
module top #(
    parameter WIDTH= 8
) (
    input clk,
    input rst,
    input [6:0] cmdin,
    input [WIDTH-1:0] din_1,
    input [WIDTH-1:0] din_2,
    input [WIDTH-1:0] din_3,
    output [WIDTH-1:0] dout_low,
    output [WIDTH-1:0] dout_high,
    output zero,
    output error
);
```

# Thank You

