

Verilog Lab I

December 2023



Basic modules

- This lab will consist on creating some basic designs (modules).
- A description of the design functionality will be provided.
- The objective is to translate the description into a synthesizable Verilog code.
- It is very important to use the module interface that will be provided.
- In order to do a syntax check on the Verilog code written, **vlogan** tool can be used.

```
vlogan -sverilog -debug_access+all verilog_file.v
```

- You can compile the simulation executable with

```
vcs -sverilog -debug_access+all verilog_file.v
```


- Then start the simulation with

```
./simv
```

Parameterized 4-input MUX

- Write the Verilog code that implements a 4-input multiplexer (mux) with variable (parameterized) input and output bus width.
- Use the following interface

 
```
1 module mux4 #(
2     parameter WIDTH= 8
3 ) (
4     input  [WIDTH-1:0] din1, din2, din3, din4,
5     input  [1:0]       select,
6     output [WIDTH-1:0] dout
7 );
```



Parameterized Register Bank

- Write the Verilog code that implements a D-type Register Bank with parameterized depth. It should:
 - Operate on positive edge of the clock (clk)
 - Have a Synchronous reset (rst)
 - Have an enable signal (wr_en) which allows data capturing only when asserted.
- Use the following interface
 
```
1 module register_bank #(
2     parameter WIDTH = 8
3 ) (
4     input  clk,
5     input  rst,
6     input  wr_en,
7     input  [WIDTH-1:0] in,
8     output [WIDTH-1:0] out
9 );
```



How to instantiate a module?

Two ways of port connection (can't be mixed)

Port connection by ordered list

```
1 module myblock ( input a, b, c
2                 output x );
3
4
5 module top ( );
6     logic a,b,c,x;
7     myblock instancia_name(
8         a,b,c,x);
9 endmodule
```


Port connection by name

```
1 module myblock ( input a, b, c
2                 output x );
3
4
5 module top ( );
6     logic P,Q,R,x_top;
7     myblock instancia_name(
8         .x(x_top),
9         .a(P),
10        .c(Q),
11        .b()
12    );
13 endmodule
```

Parameterized 4-input MUX with output register

- Write the verilog code that implements a 4-input multiplexer (mux) with a variable (parameterized) input and output bus width, and synchronous output.
- Only to learn how to instantiate modules. Will not be used later in the project.
- Use the following interface

 
```
module mux4_registered #(
    parameter WIDTH= 8
) (
    input  clk,
    input  rst,
    input  [1:0] sel,
    input  [WIDTH-1:0] in1, in2, in3, in4,
    output [WIDTH-1:0] out
);
```



Basic ALU

- Write the Verilog code for a basic ALU module (Arithmetic Logic Unit).
 - This ALU has to have addition, subtraction, multiplication and division operations.
 - It should have two variable (parameterized) width inputs and output bus in accordance.
 - Signal **zero**[0] should be asserted when the result of the current operation is 0.
 - Signal **error**[0] should be asserted when dividing by 0 is attempted or when input data is **not** valid.
 - On error condition, output must be forced to be -1
 - Operations should be described using Verilog arithmetic operators.
- Use the following interface
 
```
module ALU #(
    parameter WIDTH = 8
) (
    input  [WIDTH-1:0] in1, in2,
    input  [3:0] op,
    input  invalid_data,
    output [2*WIDTH-1:0] out,
    output zero,
    output error
);
```




Memory

- Write the Verilog code that implements a parameterized $2 \times \text{WIDTH}$ per 256 words memory.
- The memory is synchronous for writing data and asynchronous for reading data
- The memory has a pin to enable the writing and a pin to enable the reading

```
module memory #(
    parameter WIDTH = 8
) (
    input clk, memoryWrite, memoryRead,
    input [2*WIDTH-1:0] memoryWriteData,
    input [WIDTH-1:0] memoryAddress,

     output [2*WIDTH-1:0] memoryOutData
);
```



Thank You

